

QUESTION #1 :

(a) TRUTH TABLE:

	a_2	a_1	a_0	b_2	b_1	b_0
0	0	0	0	0	1	1
1	0	0	1	1	0	0
2	0	1	0	1	0	1
3	0	1	1	1	1	0
4	1	0	0	1	1	1
5	1	0	1	1	1	1
6	1	1	0	1	1	1
7	1	1	1	1	1	1

(b) Simplification for b_0 :

	\bar{a}_2	\bar{a}_1	\bar{a}_0	a_2	a_1	a_0
0	1	0	0	1		
1	1	1	1	1		

$$b_0(a_2, a_1, a_0) = a_2 + \bar{a}_0$$

Simplification for b_1 :

	\bar{a}_2	\bar{a}_1	\bar{a}_0	a_2	a_1	a_0
0	1	0	1	1		
1	1	1	1	1		


$$b_1(a_2, a_1, a_0) = a_2 + \bar{a}_1 \bar{a}_0 + a_1 a_0$$

Simplification for b_2 :

	\bar{a}_2	\bar{a}_1	\bar{a}_0	a_2	a_1	a_0
0	0	1	1	1		
1	1	1	1	1		

$$b_2(a_2, a_1, a_0) = a_2 + a_1 + a_0$$

(c) Circuit Diagram:

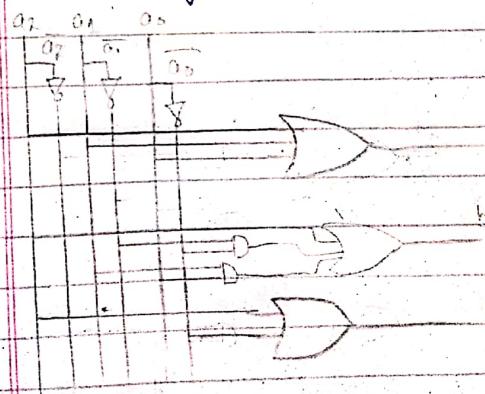

(4)

QUESTION #2

(a) TRUTH TABLE:

	a_2	a_1	a_0	out
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

(b) Simplification of out using K-maps.

	$\bar{a}_1\bar{a}_0$	\bar{a}_1a_0	$a_1\bar{a}_0$	a_1a_0
\bar{a}_2	0	0	(1)	0
a_2	0	(1)	(1)	1

$$\text{out}(a_2, a_1, a_0) = a_2a_0 + a_2a_1 + a_1a_0$$

(c) Circuit Diagram:


QUESTION #3

	P_2	P_1	P_0	out
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

	\bar{P}_1P_0	$\bar{P}_1\bar{P}_0$	P_1P_0	$P_1\bar{P}_0$
\bar{P}_2	0	0	(1)	0
P_2	0	(1)	(1)	1

$$\text{out}(P_2, P_1, P_0) = P_2P_0 + P_2P_1 + P_1P_0$$

Circuit Diagram:

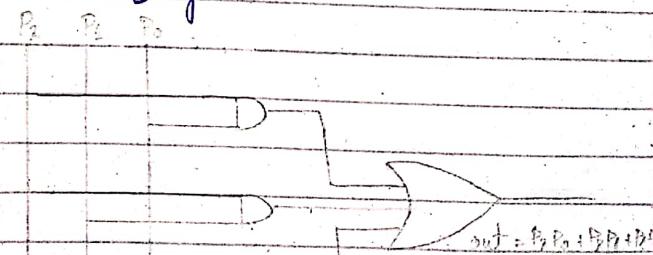

QUESTION #4:

Truth Table:

u	y	$\text{light}(u,y)$
0	0	1
0	1	0
1	0	0
1	1	1


$$\bar{u}\bar{y}$$

$$\text{light}(u,y) = \sum_m(0,3)$$

$$" = m_0 + m_3$$

$$" = \bar{u}\bar{y} + uy$$

Circuit Diagram:

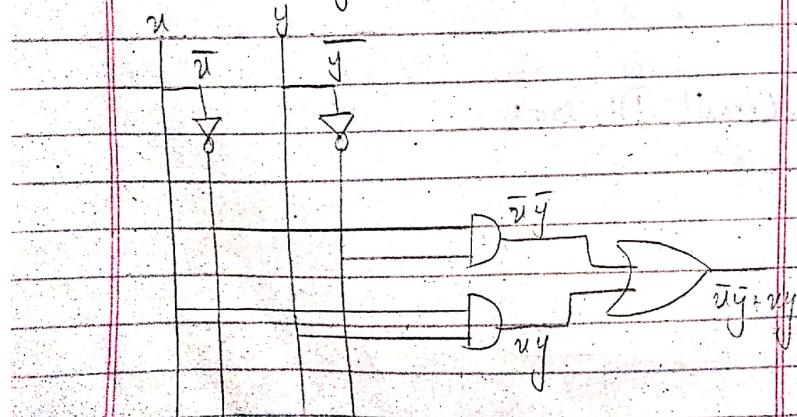

QUESTION #5:

Truth Table:

u	y	z	a_6	a_5	a_4	a_3	a_2	a_1
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

Simplification using K-Map.

a₆:

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{u}	0	0	0	0
u	0	0	(1)	(1)

$$a_6(u,y,z) = uy$$

a₄:

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz	$a_4(u,y,z) = \bar{u}yz + u\bar{y}z$
\bar{u}	0	0	(1)	0	$a_4(u,y,z) = z(\bar{u}y + u\bar{y})$
u	0	(1)	0	0	$= z(u \oplus y)$

(8)

$$a_5: \begin{array}{c} \bar{y}_2 \bar{y}_2 y_2 y_2 \\ \hline \bar{u} | 0 & 0 & 0 & 0 \\ u | 1 & 1 & 1 & 0 \end{array}$$

\bar{u}	0	0	0	0
u	1	1	1	0

$$a_5(u, y, z) = u\bar{y} + uz$$

$$a_3: \begin{array}{c} \bar{y}_2 \bar{y}_2 y_2 y_2 \\ \hline \bar{u} | 0 & 0 & 0 & 1 \\ u | 0 & 0 & 0 & 1 \end{array}$$

\bar{u}	0	0	0	1
u	0	0	0	1

$$a_3(u, y, z) = y\bar{z}$$

$$a_2: \begin{array}{c} \bar{y}_2 \bar{y}_2 y_2 y_2 \\ \hline \bar{u} | 0 & 0 & 0 & 0 \\ u | 0 & 0 & 0 & 0 \end{array}$$


\bar{u}	0	0	0	0
u	0	0	0	0

$$a_2(u, y, z) = 0$$


(9)

Circuit Diagrams


$$u \quad y \quad z$$

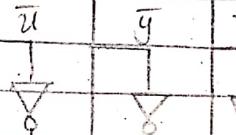


a6

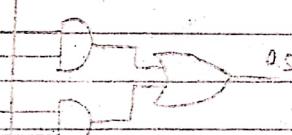

0.5

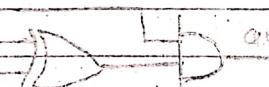

0.4

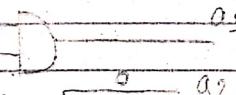

a3

a2

a1

a1:

\bar{y}_2	\bar{y}_2	y_2	y_2
\bar{u}	0	1	1
u	0	1	1

$$a_1(u, y, z) = z$$

10


QUESTION #6:

	A		B		O_{it}
	a_1	a_0	b_1	b_0	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	4	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	1

11

Circuit Diagram

a o ai ba

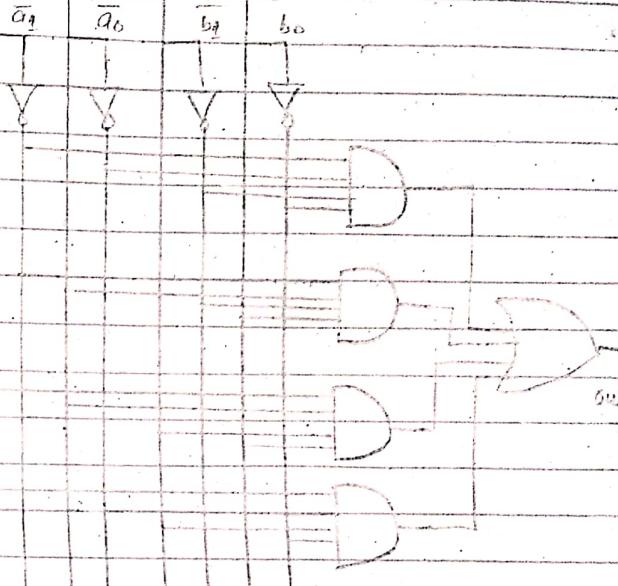

b₁bo b₁bo b₁bo b₁bo

$\bar{a}1\bar{a}0$	(1)	0	0	0	$Out = \bar{a}\bar{q}\bar{a}0\bar{b}\bar{b}\bar{b}0$
$\bar{a}1a0$	0	(1)	0	0	$\bar{a}1a0\bar{b}\bar{b}0 +$
$a\bar{q}\bar{a}0$	0	0	(1)	0	$a1a0\bar{b}\bar{b}0 +$
$a1\bar{a}0$	0	0	0	(1)	$a1\bar{a}0 + \bar{b}\bar{b}0$

(12)

QUESTION #7

w	y	u	y	z	a	b	c	d
0	0	0	0	0	0	0	0	0
1	0	0	0	1	1	1	1	1
2	0	0	1	0	1	1	1	0
3	0	0	1	1	1	1	0	1
4	0	1	0	0	1	1	0	0
5	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	0
7	0	1	1	1	1	0	0	1
8	1	0	0	0	1	0	0	0
9	1	0	0	1	0	1	1	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	0	1	0	1
12	1	1	0	0	0	1	0	0
13	1	1	0	1	0	0	1	1
14	1	1	1	0	0	0	1	0
15	1	1	1	1	0	0	0	1

Simplification using K-Map:

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{u}$	0	1	1	0
$\bar{w}u$	1	1	1	1
$w\bar{u}$	0	0	0	0
wu	1	0	0	0

(13)

$$a(w, y, z) = \bar{w}u + \bar{w}z + \bar{w}y + \bar{u}z$$

b)

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{u}$	0	1	1	1
$\bar{w}u$	1	0	0	0
$w\bar{u}$	1	0	0	0
wu	0	1	1	1

$$b(w, u, y, z) = \bar{u}y + \bar{u}z + u\bar{y}\bar{z}$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{u}$	0	1	0	1
$\bar{w}u$	0	1	0	1
$w\bar{u}$	0	1	0	1
wu	0	1	0	1

$$c(w, u, y, z) = \bar{y}z + y\bar{z}$$


	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{u}$	0	1	1	0
$\bar{w}u$	0	1	1	0
$w\bar{u}$	0	1	1	0
wu	0	1	1	0

$$d(w, y, z) = z$$

(14)

Circuit Diagram:

w u y z

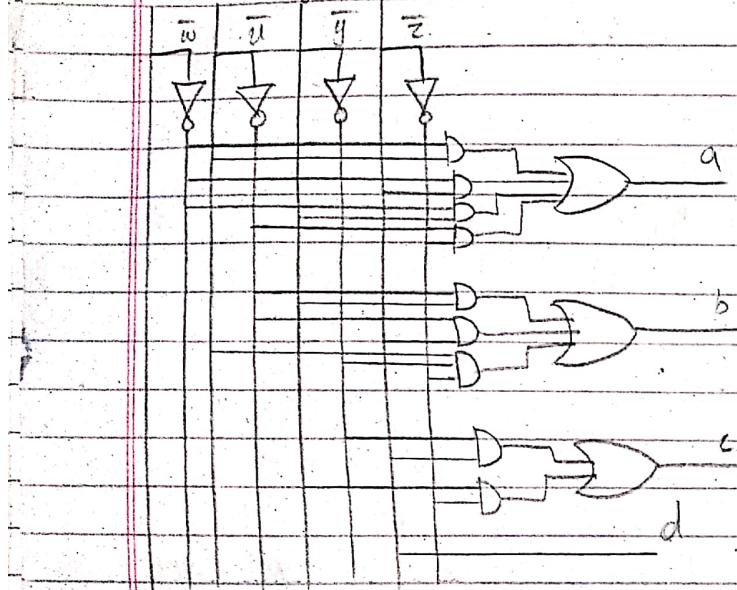

(15)


K-Map for Simplifications:

	$\bar{D}\bar{L}$	$\bar{D}L$	$D\bar{L}$	DL
\bar{T}	0	0	0	0
T	0	1	1	1

$$A(T, D, L) = TL + TD$$

Circuit Diagram:

T D L

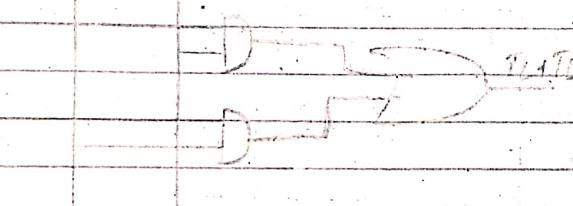QUESTION #8:

	T	D	L	A
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Night = 1

Door open = 1

laser light disturbed = 1

Day = 0

Door closed = 0

laser light not disturbed = 0

Alarm ON = 1

Alarm OFF = 0

QUESTION #9:

	w	u	y	z	out
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0

(16)


8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

 $\bar{y}\bar{z}$ $\bar{y}z$ $y\bar{z}$ yz

$\bar{w}\bar{u}$	(1)	(1)	0	(1)
$\bar{w}u$	0	0	0	0
$w\bar{u}$	0	(1)	(1)	(1)
wu	0	0	0	0

$$F(w, u, y, z) = \bar{w}\bar{u}\bar{y} + \bar{w}\bar{u}z + w\bar{u}z + wu\bar{y}$$

Circuit Diagram

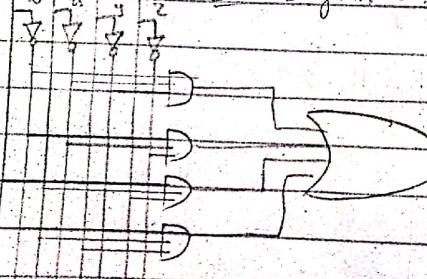

QUESTION# 10:


Truth Table:

B	F	0
0	0	0
0	1	1
1	0	1
1	1	0

F	F
0	(1)
(1)	0

$$0(B, F) = \bar{B}F + B\bar{F}$$

Circuit Diagram:

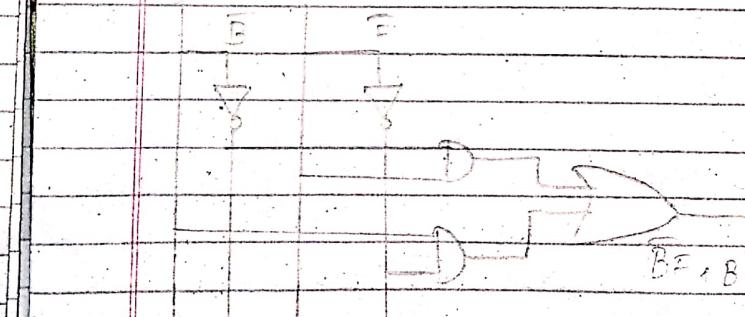

QUESTION #11:


	A	B	C	Out
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	0	(1)	0
A	0	(1)	0	(1)

$$\text{Out}(A, B, C) = \bar{A}BC + A\bar{B}C + AB\bar{C}$$

Circuit Diagram:

A B C

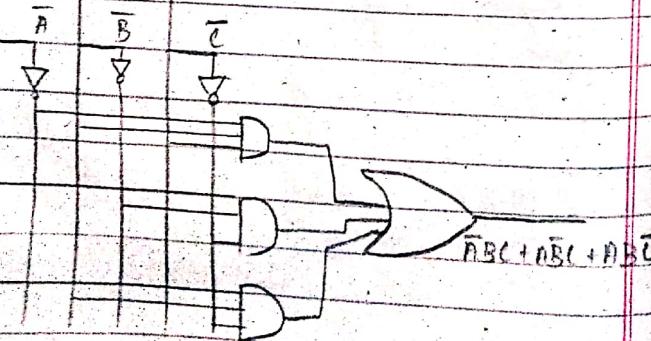

QUESTION #12:

(a) $F(u, y, z) = \Sigma_m(2, 3, 6, 7)$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{u}	0	0	1	1
u	0	0	1	1

$$F(u, y, z) = y$$

(b) $F(A, B, C, D) = \Sigma_m(7, 13, 14, 15)$

	\bar{D}	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	0	0	1	0
AB	0	1	1	1
$A\bar{B}$	0	0	0	0

$$F(A, B, C, D) = ABD + ABC + BCD$$

(c) $F(A, B, C, D) = \Sigma_m(4, 6, 7, 15)$

	\bar{D}	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	1	0	1	1
AB	0	0	1	0
$A\bar{B}$	0	0	0	0

$$F(A, B, C, D) = \bar{A}B\bar{D} + BLD$$

(2)

$$(d) F(w, u, y, z) = \text{Sum}(2, 3, 12, 13, 14, 15)$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{u}$	0	0	1	1
$\bar{w}u$	0	0	0	0
$w\bar{u}$	1	1	1	1
wu	0	0	0	0

$$F(w, u, y, z) = wu + \bar{w}\bar{u}y.$$

$$(e) F(u, y, z) = uy + \bar{u}\bar{y}\bar{z} + \bar{u}y\bar{z}$$

$$\quad\quad\quad = uy(z + \bar{z}) + \bar{u}\bar{y}\bar{z} + \bar{u}y\bar{z}$$

$$\quad\quad\quad = uy2 + uy\bar{z} + \bar{u}\bar{y}\bar{z} + \bar{u}y\bar{z}$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{u}	1	0	0	1
u	0	0	1	1

$$F(u, y, z) = \bar{u}\bar{z} + uy$$

(3)

$$(f) F(A, B, C) = \bar{A}\bar{B} + B\bar{C} + \bar{B}C$$

$$= \bar{A}\bar{B}(C + \bar{C}) + B\bar{C}(A + \bar{A}) + \bar{B}C(A + \bar{A})$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

	$\bar{B}C$	$B\bar{C}$	BC	$\bar{B}\bar{C}$
\bar{A}	1	0	1	1
A	1	0	0	1

$$F(A, B, C) = \bar{C} + \bar{A}B$$

$$(g) F(a, b, c) = \bar{a}\bar{b} + bc + \bar{a}be$$

$$= \bar{a}\bar{b}(c + \bar{c}) + bc(a + \bar{a}) + \bar{a}b\bar{c}$$

$$= \bar{a}\bar{b}c + \bar{a}\bar{b}\bar{c} + abc + \bar{a}bc + \bar{a}b\bar{c}$$

	bc	$b\bar{c}$	$\bar{b}c$	$\bar{b}\bar{c}$
\bar{a}	1	1	1	1
a	0	0	1	0

$$F(a, b, c) = \bar{a} + bc$$

22

$$(h) F(u, y, z) = u\bar{y}z + \bar{u}yz + \bar{u}\bar{y}z + u\bar{y}\bar{z}$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{u}	0	0	(1)	0
u	0	1	(1)	1

$$F(u, y, z) = u\bar{z} + u\bar{y} + y\bar{z}$$

QUESTION # 13:

$$(a) F(u, y, z) = \prod_M(0, 1, 4, 5)$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{u}	0	0	1	1
u	0	0	1	1

$$F(u, y, z) = \bar{y}$$

$$F(\bar{u}, y, z) = \bar{y} = y$$

$$(b) F(A, B, C, D) = \prod_M(0, 1, 2, 3, 4, 10, 11)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	0	1	1	1
$A\bar{B}$	1	1	0	0
AB	1	1	0	0

23

$$F(A, B, C, D) = (\bar{A}\bar{B}) + (\bar{B}C) + (\bar{D}\bar{C})$$

$$F(A, B, C, D) = (\bar{A}\bar{B}) + (\bar{B}C) + (\bar{A}\bar{C})$$

$$F(A, B, C, D) = (A+B) \cdot (B+C) \cdot (A+C+D)$$

$$(c) F(w, v, y, z) = \prod_M(1, 3, 5, 7, 13, 15)$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{w}\bar{v}$	1	0	0	1
$\bar{w}v$	1	0	0	1
$w\bar{v}$	1	0	0	1
wv	1	0	0	1

$$F(w, v, y, z) = \bar{w}z + w\bar{z}$$

$$F(w, v, y, z) = \bar{w}z + wz$$

$$F(w, v, y, z) = (w+\bar{z}) \cdot (\bar{w}+\bar{z})$$

94

QUESTION #14:

$$(a) F(u, y, z) = \bar{u}\bar{z} + \bar{y}\bar{z} + y\bar{z} - uy\bar{z}$$

	$\bar{z}\bar{y}$	$\bar{y}z$	yz	$y\bar{z}$
\bar{u}	1	0	0	1
u	1	0	1	1

$$(i) F(u, y, z) = \bar{z} + uy$$

$$(ii) F(u, y, z) = \bar{y}z + \bar{u}z$$

$$F(u, y, z) = \bar{u}z + \bar{y}z$$

$$F(u, y, z) = (u + \bar{z})(y + \bar{z})$$

$$(b) F(A, B, C, D) = (A + \bar{B} + D) \cdot (\bar{A} + B + D) \cdot (C + D) \cdot (\bar{C} + D)$$

Taking Functions complement we get

$$F(A, B, C, D) = (\bar{A}B\bar{D}) + (A\bar{B}\bar{D}) + (\bar{C}\bar{D}) + (CD)$$

Now plotting these on K-Map as (0)
and rest boxes (1).

95

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	0	1	0	1
$\bar{A}B$	0	1	0	0
$A\bar{B}$	0	1	0	1
AB	0	1	0	0

$$(i) F(A, B, C, D) = \bar{C}D + \bar{A}\bar{B}C\bar{D} + ABC\bar{D}$$

$$(ii) F(A, B, C, D) = \bar{C}\bar{D} + C\bar{D} + \bar{A}B\bar{D} + A\bar{B}\bar{D}$$

$$F(A, B, C, D) = \bar{C}\bar{D} + (C + \bar{A}B\bar{D}) + \bar{A}\bar{B}\bar{D}$$

$$F(A, B, C, D) = (C + D) \cdot (\bar{C} + \bar{D}) \cdot (A + \bar{B} + D) \\ + (\bar{A} + B + D)$$

$$(c) F(A, B, C, D) = (\bar{A} + \bar{B} + \bar{D}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{D}) \cdot (B + \bar{C} + \bar{D})$$

Taking Functions complement then
Map on K-Map for '0'

$$F(A, B, C, D) = (ABD) + (\bar{A}B\bar{C}) + (A\bar{B}D) + (\bar{B}CD)$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1	1	0	1
$\bar{A}B$	1	1	0	0
$A\bar{B}$	1	0	0	1
AB	0	0	0	0

$$(i) F(A, B, C, D) = \bar{A}\bar{C} + \bar{C}\bar{D} + A\bar{D} + \bar{B}\bar{D}$$

$$(ii) F(A, B, C, D) = AD + CD + \bar{A}\bar{B}C$$

$$F(A, B, C, D) = \bar{A}D + CD + \bar{A}BC$$

$$F(A, B, C, D) = (\bar{A} + \bar{D}) \cdot (\bar{C} + \bar{D}) \cdot (A + \bar{B} + \bar{C})$$

$$(d) F(A, B, C, D) = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D})(A + B + \bar{D}) / (A + \bar{B} + \bar{C} + \bar{D})$$

Taking functions complement and
then map on K-map for which
its '0'.

$$F(A, B, C, D) = (AB\bar{D}) + (AD) + (\bar{A}B\bar{D}) + (\bar{A}\bar{B}\bar{C}\bar{D})$$

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	0	1	1	1
$A\bar{B}$	0	0	0	0
AB	1	0	0	1

$$(i) F(ABC, D) = \bar{B}\bar{D} + \bar{A}BC + \bar{A}BD$$

$$(ii) F(A, B, C, D) = AD + \bar{B}D + ABC + B\bar{C}\bar{D}$$

$$F(H, B, L, D) = \bar{A}D + \bar{B}D + ABC + B\bar{C}\bar{D}$$

$$F(A, B, L, D) = (\bar{A} + \bar{D}) \cdot (B + \bar{D}) \cdot (\bar{A} + \bar{B} + \bar{L}) \cdot (\bar{B} + \bar{L} + \bar{D})$$

$$(e) F(V, W, U, Y) = \bar{W}Y + V\bar{U} + VWU - V\bar{W}\bar{U} + V\bar{W}Y$$

	$\bar{V}Y$	$\bar{U}Y$	UY	$V\bar{Y}$
$\bar{V}\bar{W}$	1	1	1	1
$\bar{V}W$	1	1	1	1
$V\bar{W}$	0	0	0	0
UV	1	1	1	1

$$(i) F(V, W, U, Y) = \bar{V} + \bar{W}$$

$$(ii) F(V, W, U, Y) = VW$$

$$F(V, W, U, Y) = \bar{V}\bar{W}$$