

## Homework 1

Due: Wednesday, October 19, 2022

---

- This homework is due on Wednesday, October 19, 2022.
  - Hand in your completed handwritten homework to me during our Wednesday lecture.
  - There is a 25% penalty per day for late submission.
  - Copied homework will be awarded 0 marks.
- 

1. Think of ten 3-variable functions and design circuits for them using sum-of-minterms technique.
2. Think of five 4-variable functions and design circuits for them using product-of-maxterms technique.